

Laboratory 3: Pulse Generation (5%)

A) Objectives

- To generate pulses from a constant supply.

B) Equipment

- NE555 Timer, 74HC14 Schmitt-Trigger Inverter.

C) Tinkercad Simulation Part


Reminder: Find “Breadboard Small” in Tinkercad to build each simulation circuit on it.

Simulation 1: Review of LM7805 Circuit

[Lab#03_S1]

Step 1: Create a new circuit in **Tinkercad** and change the circuit name.

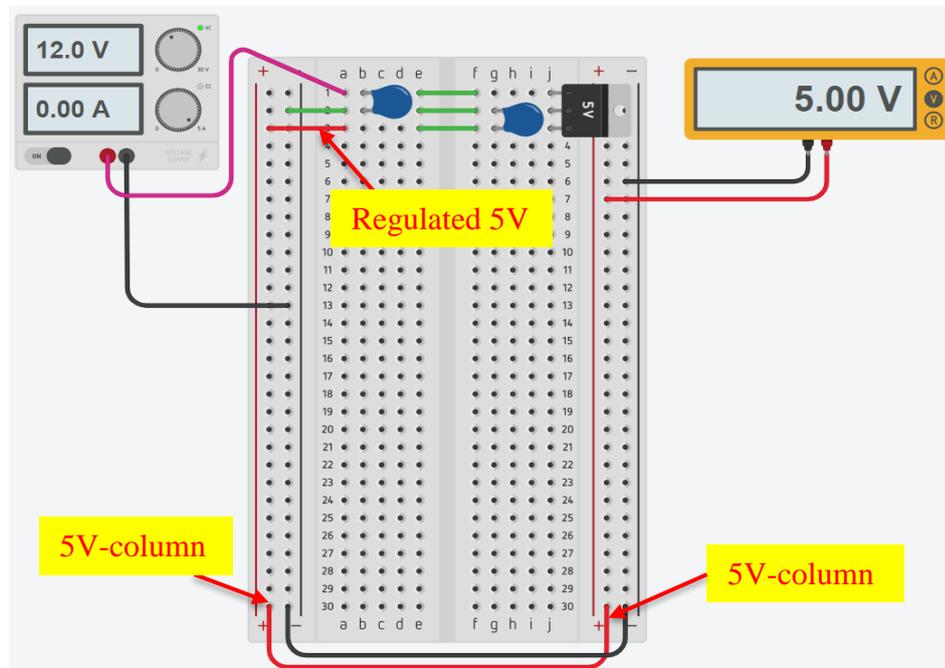Step 2: Refer to Lab#02, rebuild the LM7805 regulator circuit as below (no need of adding LED and resistor). Set the regulated 5V (output of LM7805) to both of the **5V-columns** on the breadboard.




Step 3: Use multimeter to confirm the voltage value of the **5-column** at the right side of the breadboard.

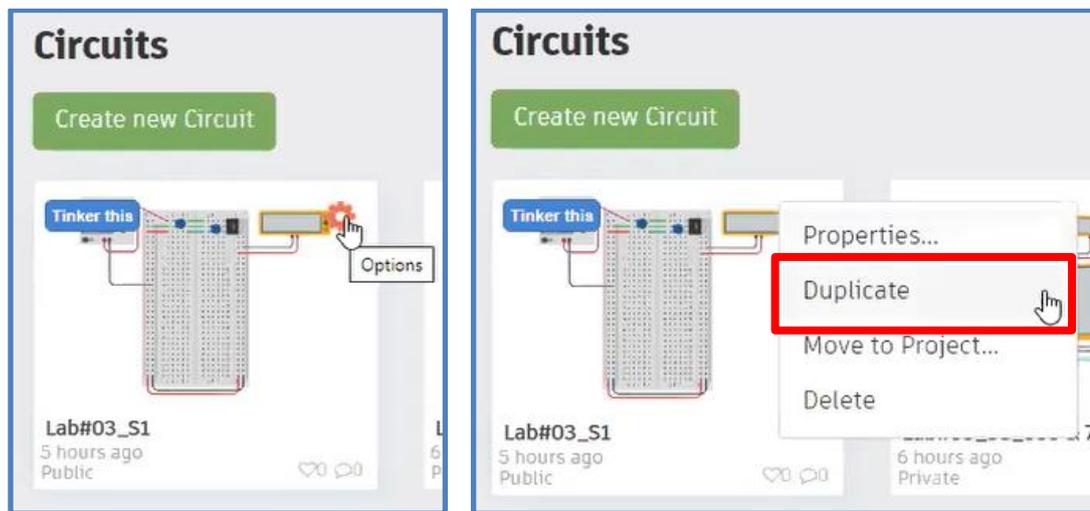
****** TA Check 1: Show your TA the multimeter reading of 5V.**

Simulation 2: Constructing a pulse generator with a NE555 Timer [Lab#03_S2]

- Step 1: Click the Tinkercad logo to go back to dashboard. You shall see your circuits thumbnail appears. The most recently revised work should be on top, i.e. your “Lab#03_S1” circuit as you just completed it in Simulation 1.
- Step 2: Move your mouse pointer over the thumbnail of “Lab#03_S1” (the re-arranged LM7805 regulator circuit), an Options icon  will appear on the top right corner. Click it and select “Duplicate”.



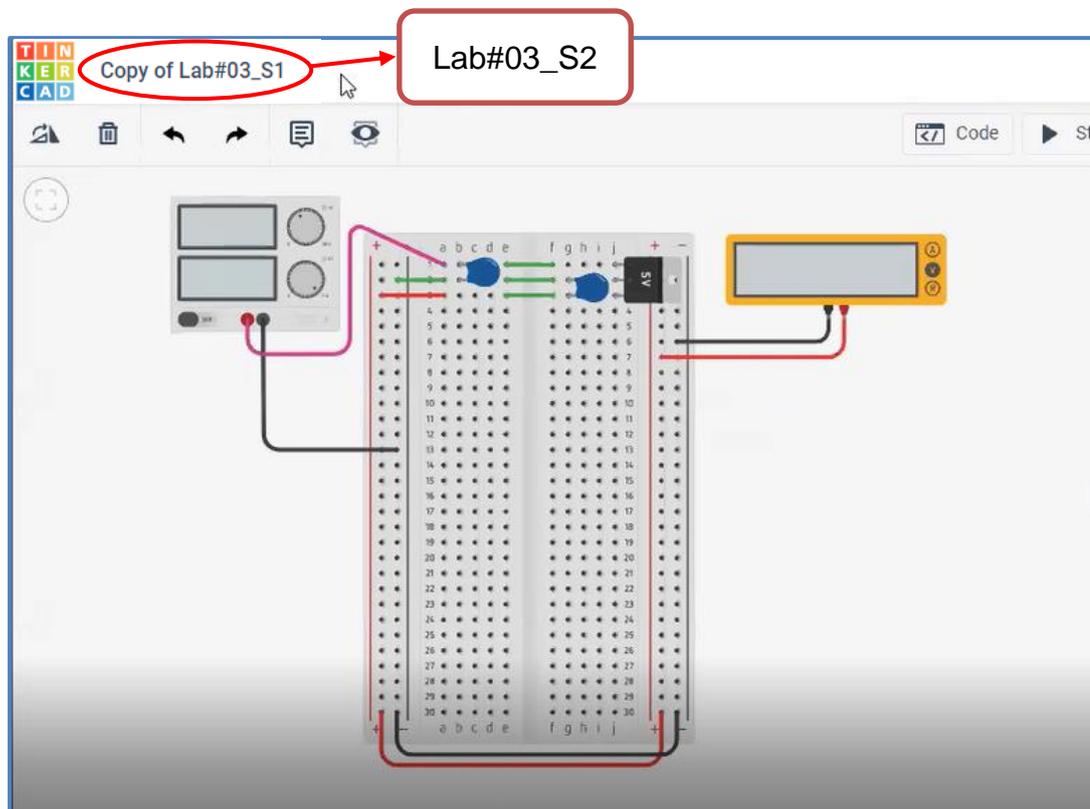- Step 3: A new circuit is created as “Copy of Lab#03_S1”. Change the circuit name to “Lab#03_S2”.




Note: For this circuit simulation, you need to put your timer circuit below the LM7805 regulator circuit on the breadboard (You may refer to Tutorial notes for the breadboard arrangement).


Step 4: Find “555 Timer” in the instrument list and construct the circuit shown below with the component values below.

$$R_A = 30\text{k}\Omega, R_B = 10\text{k}\Omega, C_1 = C_2 = C_3 = 0.1\mu\text{F}$$

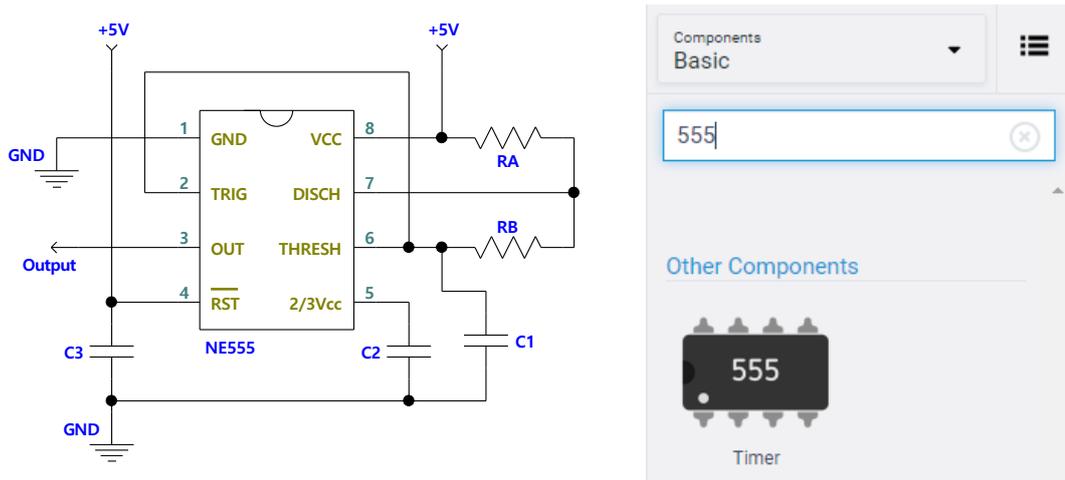Note that the 5V should be from the LM7805 regulator output, i.e. 5V-column on the breadboard.



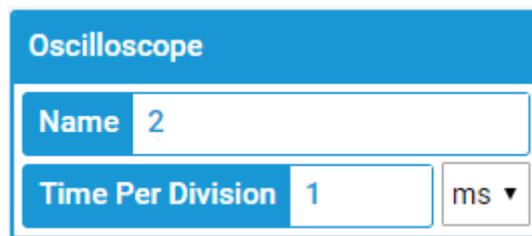Step 5: Use Oscilloscope to observe the output at pin 3 of the NE555. You may need to change the “Time Per Division” to “1ms”.



**** TA Check 2: Show the generated pulse (at least two completed periods) on Oscilloscope to your TA

Q1: With the formulae given below, what should be the theoretical (calculated) frequency and duty cycle of the pulse signal generated? (Show your calculation)

Clock High Time = $0.7 (R_A + R_B) C_1$
Clock Low Time = $0.7 (R_B) C_1$
Period = $0.7 (R_A + 2R_B) C_1$

Simulation 3: Constructing a Schmitt Trigger circuit


[Lab#03_S3]

Note: For this circuit simulation, you need to put your Schmitt Trigger circuit below the 555 Timer circuit on the breadboard (You may refer to [Tutorial notes for the breadboard arrangement](#)).


Step 1: Duplicate your “Lab#03_S2” circuit and change its name to “Lab#03_S3”.

Step 2: Find the “Potentiometer” (variable resistor) in the instruments list.

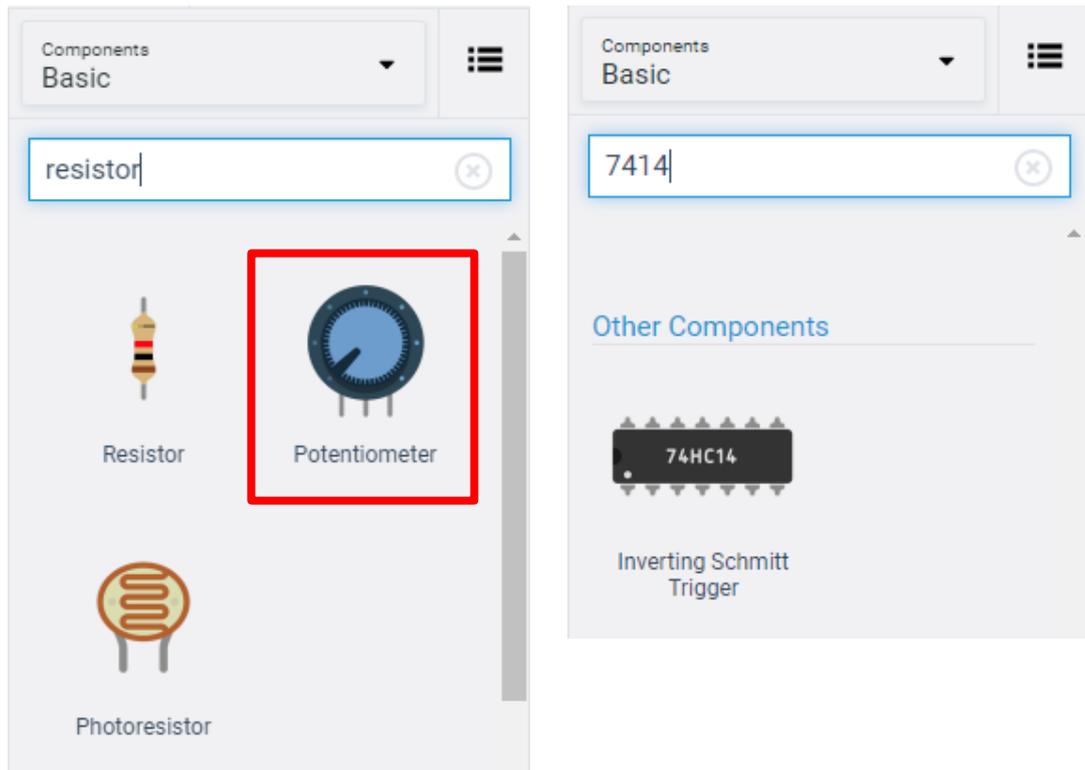Step 3: Find the 74HC14 “Inverting Schmitt Trigger” in the instruments list.



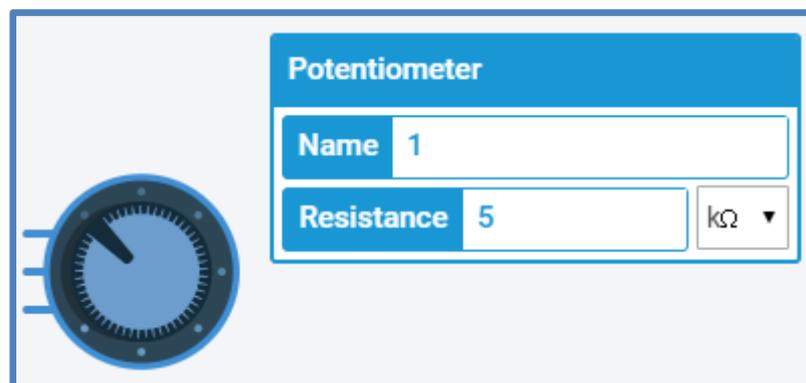
Step 4: Set the “Resistance” (total resistance) of the “Potentiometer” to 5k Ω .




Step 5: Connect the 74HC14 “Inverting Schmitt Trigger” to the timer output (Pin 3 of 555 Timer) as shown at next page.

Step 6: Replace the resistors R_A and R_B in Simulation 2 with the “Potentiometer”.

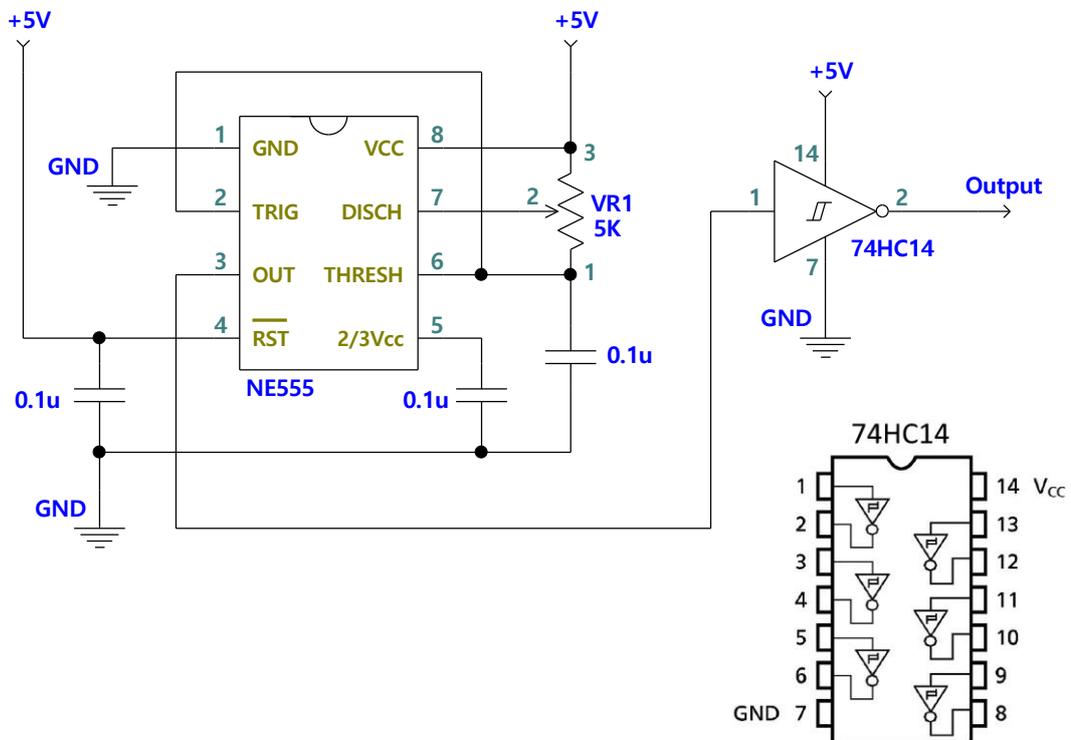Step 7: In this experiment, you need two Oscilloscopes. Use Oscilloscope 1 to measure Pin 3 of 555 Timer and Oscilloscope 2 to measure Pin 2 of 74HC14.



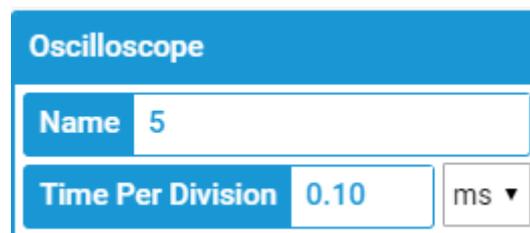Step 8: Click and turn the “Potentiometer” (variable resistor) to re-assign the resistance into the two parts, until at least two completed periods shown on the Oscilloscopes. You may need to change the “Time Per Division” to “0.1ms”.



**** TA Check 3: Demo to your TA the waves on the two Oscilloscopes (at least two completed periods).

Step 9: Notice the difference between the waveforms on Oscilloscope 1 and Oscilloscope 2. Answer below question in your summary sheet.

Q2: What is the difference between the waveforms? (indicate the function 74HC14)

Remember to change the circuit names and copy share links of your Simulations 1-3 to the table in your summary sheet.